

Логичко пројектовање

Предавање 6/10

**Опис секвенцијалних
мрежа у VHDL-у**


Увод

- У овој лекцији се врши моделовање секвенцијалних мрежа коришћењем VHDL техника представљених у претходној лекцији.
- VHDL моделовање секвенијалних меморијских елемената.
- VHDL моделовање коначних аутомата.
- VHDL моделовање регистара за трансфер података.
- Разумевање како се VHDL користи за креирање понашања секвенцијалних дигиталних система.



D-флип-флоп

 Example: Behavioral Model of a D-Flip-Flop in VHDL



Clk	D	Q	Qn	
0	X	Last Q	Last Qn	Store
1	X	Last Q	Last Qn	Store
┐	0	0	1	Update
┐	1	1	0	Update

```

library IEEE;
use IEEE.std_logic_1164.all;


entity Dflipflop is
    port (Clock      : in  std_logic;
          D          : in  std_logic;
          Q, Qn      : out std_logic);
end entity;

architecture Dflipflop_arch of Dflipflop is
    begin
        D_FLIP_FLOP : process (Clock)
        _begin
            if (Clock'event and Clock='1') then
                Q <= D;   Qn <= not D;
            end if;
        end process;
    end architecture;

```

D-флип-флоп са асин. ресетом

 Example: Behavioral Model of a D-Flip-Flop with Asynchronous Reset in VHDL



\bar{R}	Clk	D	Q	Qn	
0	X	X	0	1	Reset
1	0	X	Last Q	Last Qn	Store
1	1	X	Last Q	Last Qn	Store
1	\neg	0	0	1	Update
1	\neg	1	1	0	Update

```


library IEEE;
use IEEE.std_logic_1164.all;

entity Dflipflop is
    port (Clock      : in  std_logic;
          Reset      : in  std_logic;
          D          : in  std_logic;
          Q, Qn      : out std_logic);
end entity;

architecture Dflipflop_arch of Dflipflop is
begin
    D_FLIP_FLOP : process (Clock, Reset)
    begin
        if (Reset = '0') then
            Q <= '0'; Qn <= '1';
        elsif (Clock'event and Clock='1') then
            Q <= D;   Qn <= not D;
        end if;
    end process;
end architecture;
  
```

D-флип-флоп са асин. ресетом и пресетом

 Example: Behavioral Model of a D-Flip-Flop with Asynchronous Reset and Preset in VHDL



R	P	Clk	D	Q	Qn	
0	X	X	X	0	1	Reset
1	0	X	X	1	0	Preset
1	1	0	X	Last Q	Last Qn	Store
1	1	1	X	Last Q	Last Qn	Store
1	1	⌊	0	0	1	Update
1	1	⌊	1	1	0	Update

```


library IEEE;
use IEEE.std_logic_1164.all;

entity Dflipflop is
    port (Clock      : in  std_logic;
          Reset, Preset : in  std_logic;
          D           : in  std_logic;
          Q, Qn       : out std_logic);
end entity;

architecture Dflipflop_arch of Dflipflop is
begin
    D_FLIP_FLOP : process (Clock, Reset, Preset)
    begin
        if (Reset = '0') then
            Q <= '0'; Qn <= '1';
        elsif (Preset = '0') then
            Q <= '1'; Qn <= '0';
        elsif (Clock'event and Clock='1') then
            Q <= D;   Qn <= not D;
        end if;
    end process;
end architecture;
    
```

D-флип-флоп са синх. Enable

 Example: Behavioral Model of a D-Flip-Flop with Synchronous Enable in VHDL



\bar{R}	\bar{P}	Clk	EN	D	Q	Qn	
0	X	X	X	X	0	1	Reset
1	0	X	X	X	1	0	Preset
1	1	0	X	X	Last Q	Last Qn	Store
1	1	1	X	X	Last Q	Last Qn	Store
1	1	⏏	0	X	Last Q	Last Qn	Disabled (ignore clock)
1	1	⏏	1	0	0	1	Update
1	1	⏏	1	1	1	0	Update

```

library IEEE;
use IEEE.std_logic_1164.all;

entity Dflipflop is
    port (Clock      : in  std_logic;
          Reset, Preset : in  std_logic;
          D, EN      : in  std_logic;
          Q, Qn      : out std_logic);
end entity;

architecture Dflipflop_arch of Dflipflop is
    begin
        D_FLIP_FLOP : process (Clock, Reset, Preset)
        begin
            if (Reset = '0') then
                Q <= '0'; Qn <= '1';
            elsif (Preset = '0') then
                Q <= '1'; Qn <= '0';
            elsif (Clock'event and Clock='1') then
                if (EN = '1') then
                    Q <= D;  Qn <= not D;
                end if;
            end if;
        end process;
    end architecture;

```

A nested if/then statement is used to model the synchronous enable.

Моделовање коначних аутомата у VHDL-у


- Коначни аутомати могу се лако моделовати коришћењем конструкција описа понашања из претходне лекције.
- Најчешћа пракса моделирања за FSM је креирање новог кориснички дефинисаног типа који може да преузме описна имена стања из дијаграма стања.
- Затим се креирају два сигнала овог типа, `current_state` и `next_state`.
- Једном када су ови сигнали креирани, сви функционални блокови у коначном аутомату могу да користе описна имена стања у њиховим условним додељивањима сигнала.
- Логичка синтеза ће аутоматски доделити кодове стања на основу технологије која се користи (нпр. `binary`, `gray code`, `one-hot`).
- У оквиру VHDL модела коначног аутомата, користе се 3 процеса за описивање сваког од функционалних блокова, меморије стања, логике следећег стања и излазне логике.
- Да би се испитало како да моделујемо аутомат користимо пример push дугмета (пример контролера прозора из претходне лекције).
-

Моделовање коначних аутомата у VHDL-у (пример)


Example: Push-Button Window Controller in VHDL – Design Description

The window controller will send the appropriate control signals to a motor to open or close it whenever a button is pressed. The system must keep track whether the window is open or closed in order to send the correct signal, thus a state machine is needed. The block diagram and state diagram for this system is shown below.

Block Diagram

 


State Diagram

 

Моделовање коначних аутомата у VHDL-у (пример 2. део)

 Example: Push-Button Window Controller in VHDL – Entity Definition



```
library IEEE;  
use IEEE.std_logic_1164.all;  
  
entity PBWC is  
  port (Clock, Reset      : in  std_logic;  
        Press             : in  std_logic;  
        Open_CW, Close_CCW : out std_logic);  
end entity;
```

Моделовање стања

- Први корак је креирање новог кориснички дефинисаног, набројивог типа података који може да има вредности које одговарају описним именима стања.
- Имена стања узимао из дијаграма стања (w_closed и w_open).
- Ово је постигнуто декларисањем новог типа пре почетка наредбе у архитектури са кључном речи "type".
- За овај пример, креираћемо нови тип под називом State_Type и експлицитно набројиве вредности које може да узме овај тип.
- Затим креирамо два нова сигнала названа current_state и next_state. Ова два сигнала ће се користити у целом VHDL моделу.
- Следећа синтакса показује како декларисати нови тип и сигнале current_state и next_state:

```
type State_Type is (w_closed, w_open);
```

- ```
signal current_state, next_state : State_Type;
```

## Процес меморије стања

- Овај процес моделира понашање D-флип-флопова у FSM-у који задржавају вредности стања на Q излазима.
- Сваки пут када постоји растућа ивица clock-а, тренутно стање се ажурира са следећом вредношћу стања присутном на D улазима D-флип-флопова.
- Овај процес такође мора да моделира стање ресетовања.
- За пример push дугмета аутомат ће прећи у стање w\_closed када се потврди ресетовање.
- У свим другим случајевима, процес ће једноставно ажурирати current\_state са next\_state на свакоу улазну ивицу clock-а.
- Модел процеса је веома сличан моделу D-флип-флопа. Ово је очекивано јер ће се овај процес синтетизовати у један или више D-флип-флопа за задржавање тренутног стања.
- Листа осетљивости садржи само Clock и Reset и додељивање се врши само за сигнал current\_state.
- Следећи пример показује како се моделује меморија стања овог FSM-а:

```
STATE_MEMORY : process (Clock, Reset)
begin
 if (Reset = '0') then
 current_state <= w_closed;
 elsif (Clock'event and Clock='1') then
 current_state <= next_state;
 end if;
end process;
```

## Процес следећег стања

- Логика следећег стања је комбинациона логика; стога морамо укључити све улазне сигнале који се користе за генерисање следећег стања у листу осетљивости процеса.
- Сигнал `current_state` ће увек бити укључен у листу осетљивости за процес следећег стања поред свих улаза у систем.
- На пример, систем има још један улаз који се зове `Press`. Овај процес креира доделе сигналу `next_state`.
- Уобичајено је користити `case` наредбу са доделама за сваки излаз посебно.
- У сваком стању у оквиру `case` наредбе, користи се `if/else` наредба за моделовање доделе за различите улазе за `Press`.
- Следећи пример показује како се моделује логика следећег стања стања за пример FSM-a.

```

NEXT_STATE_LOGIC : process (current_state, Press)
begin
 case (current_state) is
 when w_closed => if (Press = '1') then
 next_state <= w_open;
 else
 next_state <= w_closed;
 end if;
 when w_open => if (Press = '1') then
 next_state <= w_closed;
 else
 next_state <= w_open;
 end if;
 when others => next_state <= w_closed;
 end case;
end process;

```

## Процес излазне логике

- Излазна логика је комбинациона логика, стога морамо укључити све улазне сигнале који учествују у генерисању излаза.
- Current\_state сигнали ће увек бити укључени у листу осетљивости.
- Ако је аутомат Милијевог типа, тада ће и улази бити укључени у листу осетљивости. Ако је аутомат Муровог типа, онда ће само Current\_state сигнали бити укључени у листу осетљивости.
- Пример Press дугмета је аутомат Милијевог типа, тако да улаз Press треба да буде укључен у листу осетљивости.
- Овај процес има доделе само за излазе аутомата (Open\_CW и Close\_CCW).
- Следећи пример показује како се моделује излазна логика за пример FSM-a.

```

OUTPUT_LOGIC : process (current_state, Press)
begin
 case (current_state) is
 when w_closed => if (Press = '1') then
 Open_CW <= '1'; Close_CCW <= '0';
 else
 Open_CW <= '0'; Close_CCW <= '0';
 end if;

 when w_open => if (Press = '1') then
 Open_CW <= '0'; Close_CCW <= '1';
 else
 Open_CW <= '0'; Close_CCW <= '0';
 end if;

 when others => Open_CW <= '0'; Close_CCW <=
 '0';
 end case;
end process;
```

## Процес излазне логике

- Излазна логика је комбинациона логика, стога морамо укључити све улазне сигнале који учествују у генерисању излаза.
- Current\_state сигнали ће увек бити укључени у листу осетљивости.
- Ако је аутомат Милијевог типа, тада ће и улази бити укључени у листу осетљивости. Ако је аутомат Муровог типа, онда ће само Current\_state сигнали бити укључени у листу осетљивости.
- Пример Press дугмета је аутомат Милијевог типа, тако да улаз Press треба да буде укључен у листу осетљивости.
- Овај процес има доделе само за излазе аутомата (Open\_CW и Close\_CCW).
- Следећи пример показује како се моделује излазна логика за пример FSM-a.

```

OUTPUT_LOGIC : process (current_state, Press)
begin
 case (current_state) is
 when w_closed => if (Press = '1') then
 Open_CW <= '1'; Close_CCW <= '0';
 else
 Open_CW <= '0'; Close_CCW <= '0';
 end if;

 when w_open => if (Press = '1') then
 Open_CW <= '0'; Close_CCW <= '1';
 else
 Open_CW <= '0'; Close_CCW <= '0';
 end if;

 when others => Open_CW <= '0'; Close_CCW <=
 '0';
 end case;
end process;
```

# Моделовање коначних аутомата у VHDL-у (пример 3. део)

## Example: Push-Button Window Controller in VHDL – Architecture

```
architecture PBWC_arch of PBWC is
```

```
 type State_Type is (w_closed, w_open);
 signal current_state, next_state : State_Type;
```

Declaration of user defined type for the signals current\_state and next\_state.

```
begin
```

```
 STATE_MEMORY : process (Clock, Reset)
```

The first process is used to model the state memory.

```
 begin
 if (Reset = '0') then
 current_state <= w_closed;
 elsif (Clock'event and Clock='1') then
 current_state <= next_state;
 end if;
 end process;
```

```
 NEXT_STATE_LOGIC : process (current_state, Press)
```

The second process is used to model the next state logic.

```
 begin
 case (current_state) is
 when w_closed => if (Press = '1') then
 next_state <= w_open;
 else
 next_state <= w_closed;
 end if;
 when w_open => if (Press = '1') then
 next_state <= w_closed;
 else
 next_state <= w_open;
 end if;
 when others => next_state <= w_closed;
 end case;
 end process;
```

```
 OUTPUT_LOGIC : process (current_state, Press)
```

The third process is used to output the state.

```
 begin
```

```
 case (current_state) is
```

```
 when w_closed => if (Press = '1') then
 Open_CW <= '1'; Close_CCW <= '0';
 else
 Open_CW <= '0'; Close_CCW <= '0';
 end if;
```

```
 when w_open => if (Press = '1') then
 Open_CW <= '0'; Close_CCW <= '1';
 else
 Open_CW <= '0'; Close_CCW <= '0';
 end if;
```

```
 when others => Open_CW <= '0'; Close_CCW <= '0';
```

```
 end case;
```

```
 end process;
```

```
end architecture;
```

## Експлицитно дефинисање кодирање стања са Subtypes

```
subtype State_Type is std_logic;
constant w_open : State_Type := '0';
constant w_closed : State_Type := '1';
signal current_state, next_state : State_Type;
```




# Серијски бит детектор секвенце у VHDL-у


## Example: Serial Bit Sequence Detector in VHDL – Design Description and Entity Definition

This circuit will monitor an incoming serial bit stream. The information in the bit stream represents data in groups of 3-bits. The code "111" represents that an error has occurred in the transmitter. The FSM will monitor the incoming bit stream and assert a signal called "ERR" if the sequence "111" is detected. At all other times ERR=0.


### Timing Diagram

 

### State Diagram

 

### Entity Definition

 

```

library IEEE;
use IEEE.std_logic_1164.all;

entity Seq_Det is
 port (Clock, Reset : in std_logic;
 Din : in std_logic;
 ERR : out std_logic);
end entity;

```

## Example: Serial Bit Sequence Detector in VHDL – Architecture

```

architecture Seq_Det_arch of Seq_Det is
 type State_Type is (Start, D0_is_1, D1_is_1, D0_not_1, D1_not_1);
 signal current_state, next_state : State_Type;
begin

 STATE_MEMORY : process (Clock, Reset)
 begin
 if (Reset = '0') then
 current_state <= Start;
 elsif (Clock'event and Clock='1') then
 current_state <= next_state;
 end if;
 end process;

 NEXT_STATE_LOGIC : process (current_state, Din)
 begin
 case (current_state) is
 when Start => if (Din = '1') then
 next_state <= D0_is_1;
 else
 next_state <= D0_not_1;
 end if;
 when D0_is_1 => if (Din = '1') then
 next_state <= D1_is_1;
 else
 next_state <= D1_not_1;
 end if;
 when D1_is_1 => next_state <= Start;
 when D0_not_1 => next_state <= Start;
 when D1_not_1 => next_state <= Start;
 when others => next_state <= Start;
 end case;
 end process;

 OUTPUT_LOGIC : process (current_state, Din)
 begin
 case (current_state) is
 when D1_is_1 => if (Din = '1') then
 ERR <= '1';
 else
 ERR <= '0';
 end if;
 when others => ERR <= '0';
 end case;
 end process;
end architecture;

```

Declaration of user defined type for the signals current\_state and next\_state.

Note that in this example there are states decisions that don't require if/then statements.


This is a Mealy machine so both the current state and the system inputs are present in the sensitivity list.

# 2-битни бинарни кружни бројач навише/наниже у VHDL-у

## Example: 2-Bit Binary Up/Down Counter in VHDL – Design Description and Entity Definition


This system will output a synchronous, 2-bit, binary counter. When the system input Up=1, the system will count up. When Up=0, the system will count down. The output of the counter is called CNT.

State Diagram

 

## Entity Definition

Counter\_2bit\_UpDown.vhd

 

```

library IEEE;
use IEEE.std_logic_1164.all;

entity Counter_2bit_UpDown is
port (Clock : in std_logic;
 Reset : in std_logic;
 Up : in std_logic;
 CNT : out std_logic_vector(1 downto 0));
end entity;

```

## Example: 2-Bit Binary Up/Down Counter in VHDL – Architecture (Three Process Model)

```

library IEEE;
use IEEE.std_logic_1164.all;

entity Counter_2bit_UpDown is
port (Clock, Reset : in std_logic;
 Up : in std_logic;
 CNT : out std_logic_vector(1 downto 0));
end entity;

architecture Counter_2bit_UpDown_arch of Counter_2bit_UpDown is
type State_Type is (C0, C1, C2, C3);
signal current_state, next_state : State_Type;

begin

 STATE_MEMORY : process (Clock, Reset)
 begin
 if (Reset = '0') then
 current_state <= C0;
 elsif (Clock'event and Clock='1') then
 current_state <= next_state;
 end if;
 end process;

 NEXT_STATE_LOGIC : process (current_state, Up)
 begin
 case (current_state) is
 when C0 => if (Up = '1') then
 next_state <= C1;
 else
 next_state <= C3;
 end if;
 when C1 => if (Up = '1') then
 next_state <= C2;
 else
 next_state <= C0;
 end if;
 when C2 => if (Up = '1') then
 next_state <= C3;
 else
 next_state <= C1;
 end if;
 when C3 => if (Up = '1') then
 next_state <= C0;
 else
 next_state <= C2;
 end if;
 when others => next_state <= C0;
 end case;
 end process;

 OUTPUT_LOGIC : process (current_state)
 begin
 case (current_state) is
 when C0 => CNT <= "00";
 when C1 => CNT <= "01";
 when C2 => CNT <= "10";
 when C3 => CNT <= "11";
 when others => CNT <= "00";
 end case;
 end process;
end architecture;

```

A counter is a Moore machine  
so the output only depends on  
the current state.

# Бројач у VHDL-у - тип UNSIGNED

## Example: 4-Bit Binary Up Counter in VHDL Using the Type UNSIGNED

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity Counter_4bit_Up is
 port (Clock, Reset : in std_logic;
 CNT : out unsigned(3 downto 0));
end entity;
```

The numeric\_std package is needed to include the "+" operator. This operator only works on types signed/unsigned, so we will define the output CNT as type unsigned.

```
architecture Counter_4bit_Up_arch of Counter_4bit_Up is
```

```
 signal CNT_tmp : unsigned(3 downto 0);
```

```
begin
```

```
 COUNTER : process (Clock, Reset)
```

```
 begin
```

```
 if (Reset = '0') then
```

```
 CNT_tmp <= "0000";
```

```
 elsif (Clock'event and Clock='1') then
```

```
 CNT_tmp <= CNT_tmp + 1;
```

```
 end if;
```


```
 end process;
```

```
 CNT <= CNT_tmp;
```

```
end architecture;
```

An internal signal is needed to support assignments in the form  $C \leq C+1$ ; because a port cannot be used as an argument in a signal assignment.

 A concurrent signal assignment is used to continually assign CNT\_tmp to CNT.



The counter increments on each rising edge of clock.

When the counter reaches "1111", it rolls over to "0000" and continues.



# Бројач у VHDL-у - тип INTEGER

## Example: 4-Bit Binary Up Counter in VHDL Using the Type INTEGER

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all; ← The numeric_std package contains the "+"
 operator for type integer and a conversion
 from type integer to type unsigned.

entity Counter_4bit_Up is
port (Clock, Reset: in std_logic;
 CNT : out unsigned(3 downto 0)); ← In this example, the output
end entity; port is defined to be of type
 unsigned.

architecture Counter_4bit_Up_arch of Counter_4bit_Up is

 signal CNT_int : integer; ← An internal signal of type integer
 is declared to model the counter
 functionality.


begin

 COUNTER : process (Clock, Reset)
 begin
 if (Reset = '0') then
 CNT_int <= 0;
 elsif (Clock'event and Clock='1') then

 if (CNT_int = 15) then ← A nested if/then statement checks
 CNT_int <= 0; to see if the integer counter has
 else reached its maximum value.
 CNT_int <= CNT_int + 1;
 end if;

 end if;
 end process;

  CNT <= to_unsigned(CNT_int, 4); ← A concurrent assignment between the
 internal counter and the output port is
 made that contains the conversion
 between type integer and unsigned. The 4
 in this function represents the number of
 unsigned bits to convert the integer into.
 end architecture;
```



The std\_logic\_vector is treated as unsigned and will roll over once it gets to "1111".

# Бројач у VHDL-у - тип STD\_LOGIC\_VECTOR

Example: 4-Bit Binary Up Counter in VHDL Using the Type STD\_LOGIC\_VECTOR (1)

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;
use IEEE.numeric_std_unsigned.all; ← Including this package will
 treat all std_logic_vector
 types as unsigned numbers.

entity Counter_4bit_Up is
 port (Clock, Reset : in std_logic;
 CNT : out std_logic_vector(3 downto 0)); ← The output port is
 defined to be of type
 std_logic_vector.
end entity;

architecture Counter_4bit_Up_arch of Counter_4bit_Up is


 signal CNT_std : std_logic_vector(3 downto 0); ← The internal signal to
 model the counter
 behavior is declared as
 type std_logic_vector.

begin

 COUNTER : process (Clock, Reset)
 begin
 if (Reset = '0') then
 CNT_std <= "0000";
 elsif (Clock'event and Clock='1') then
 CNT_std <= CNT_std + 1; ← No boundary checking is needed
 since the 4-bit std_logic_vector will
 simply roll over.
 end if;
 end process;

 CNT <= CNT_std; ← No type conversion is needed since the
 internal signal and output port are of type
 std_logic_vector.


end architecture;
```

 

The std\_logic\_vector is treated as unsigned and will roll over once it gets to "1111".

# Регистри у VHDL-у
 
## Example: RTL Model of an 8-Bit Register in VHDL



| $\bar{R}$ | Clk | EN | Reg_Out      |
|-----------|-----|----|--------------|
| 0         | X   | X  | x"00"        |
| 1         | X   | 0  | Last Reg_Out |
| 1         | 0   | 1  | Last Reg_Out |
| 1         | 1   | 1  | Last Reg_Out |
| 1         | 1   | 1  | Reg_In       |

Reset  
Disabled (ignore clock)  
Store  
Store  
Update


```
library IEEE;
use IEEE.std_logic_1164.all;

entity reg is
 port (Clock : in std_logic;
 Reset : in std_logic;
 Reg_In : in std_logic_vector(7 downto 0);
 EN : in std_logic;
 Reg_Out : out std_logic_vector(7 downto 0));
end entity;

architecture reg_arch of reg is
begin
 Reg_Proc : process (Clock, Reset)
 begin
 if (Reset = '0') then
 Reg_Out <= x"00";
 elsif (Clock'event and Clock='1') then
 if (EN = '1') then
 Reg_Out <= Reg_In;
 end if;
 end if;
 end process;
end architecture;
```

# Shift регистри у VHDL-у

 Example: RTL Model of a 4-Stage, 8-Bit Shift Register in VHDL



```
library IEEE;
use IEEE.std_logic_1164.all;

entity Shift_Register is
 port (Clock, Reset : in std_logic;
 Din : in std_logic_vector(7 downto 0);
 Dout0, Dout1 : out std_logic_vector(7 downto 0);
 Dout2, Dout3 : out std_logic_vector(7 downto 0));
end entity;

architecture Shift_Register_arch of Shift_Register is

 signal D0, D1, D2, D3 : std_logic_vector(7 downto 0);

begin

 SHIFT : process (Clock, Reset)
 begin
 if (Reset = '0') then
 D0 <= x"00"; D1 <= x"00"; D2 <= x"00"; D3 <= x"00";
 elsif (Clock'event and Clock='1') then
 D0 <= Din; D1 <= D0; D2 <= D1; D3 <= D2;
 end if;
 end process;

 Dout3 <= D3; Dout2 <= D2; Dout1 <= D1; Dout0 <= D0;

end architecture;
```